

Lab 5: Binary counter



EUROPEAN UNION
European Structural and Investment Funds
Operational Programme Research,
Development and Education




The Study of Modern and Developing Engineering BUT

CZ.02.2.69/0.0/0.0/18_056/0013325

Learning objectives

 The purpose of this laboratory exercise is to become familiar with the creation of sequential processes in VHDL, next to implement a clock enable signal to drive another logic with slower clock, and to design a binary counter.



Preparation tasks (done before the lab at home)

The Nexys A7 board provides five push buttons for user applications. See schematic or reference manual of the Nexys A7 board and find out the connection of these push buttons, ie to which FPGA pins are connected and how (schema). What logic/voltage value do the buttons generate when not pressed and what value when the buttons are pressed?

Calculate how many periods of clock signal with frequency of 100 MHz contain time intervals 2 ms, 4 ms, 10 ms, 250 ms, 500 ms, and 1 s. Write values in decimal, binary, and hexadecimal forms.

$$T_{clk} = \frac{1}{f_{clk}} =$$


Time interval	Number of clk periods	Number of clk periods in hex	Number of clk periods in binary
2 ms	200 000	x"3_0d40"	b"0011_0000_1101_0100_0000"
4 ms			
10 ms			
250 ms			
500 ms			
1 sec	100 000 000	x"5F5_E100"	b"0101_1111_0101_1110_0001_0000_0000"

Part 1: Synchronize repositories and create a new folder

Run Git Bash (Windows) or Terminal (Linux), navigate to your working directory, and update local repository. Create a new working folder `Labs/05-counter` for this laboratory exercise.

 Part 2: VHDL code for clock enable

To drive another logic in the design (with slower clock), it is better to generate a **clock enable signal** instead of creating another clock domain (using clock dividers) that would cause timing issues or clock domain crossing problems such as metastability, data loss, and data incoherency.



The figure above was created in [WaveDrom](#) digital timing diagram online tool. The figure source code is as follows (ticks -1, 10, 11 and 12 were manually adjusted afterwards):


```
{
  signal:
  [
    {name: "clk", wave: 'P.....'},
    {name: "ce_o", wave: '1h1.....h1'}],
  head:
  {
    tick: -1,
  },
  foot:
  {
    text: 'g_MAX = 10',
  },
}
```

Perform the following steps to simulate the clock enable circuit.

1. Create a new Vivado RTL project `counter` in your `Labs/05-counter` working folder.
2. Create a VHDL source file `clock_enable` for the clock enable circuit.
3. Choose default board: `Nexys A7-50T`.

- Open the [Clock enable circuit example](#) and copy/paste the `design.vhd` code to your `clock_enable.vhd` file. Take a look at the new parts of the VHDL source code, such as package for arithmetic operations, `generic` part, internal signal, and [synchronous process](#). **Generic** allows us to pass information into an entity and component. Since a generic cannot be modified inside the architecture, it is like a constant.
- Create a simulation source `tb_clock_enable`, copy/paste the `testbench.vhd` code and run the simulation. Verify the meaning of the constant `c_MAX` and reset generation process.

The default simulation run time is set to 1000 ns in Vivado. You can change it in the menu **Tools > Settings...**

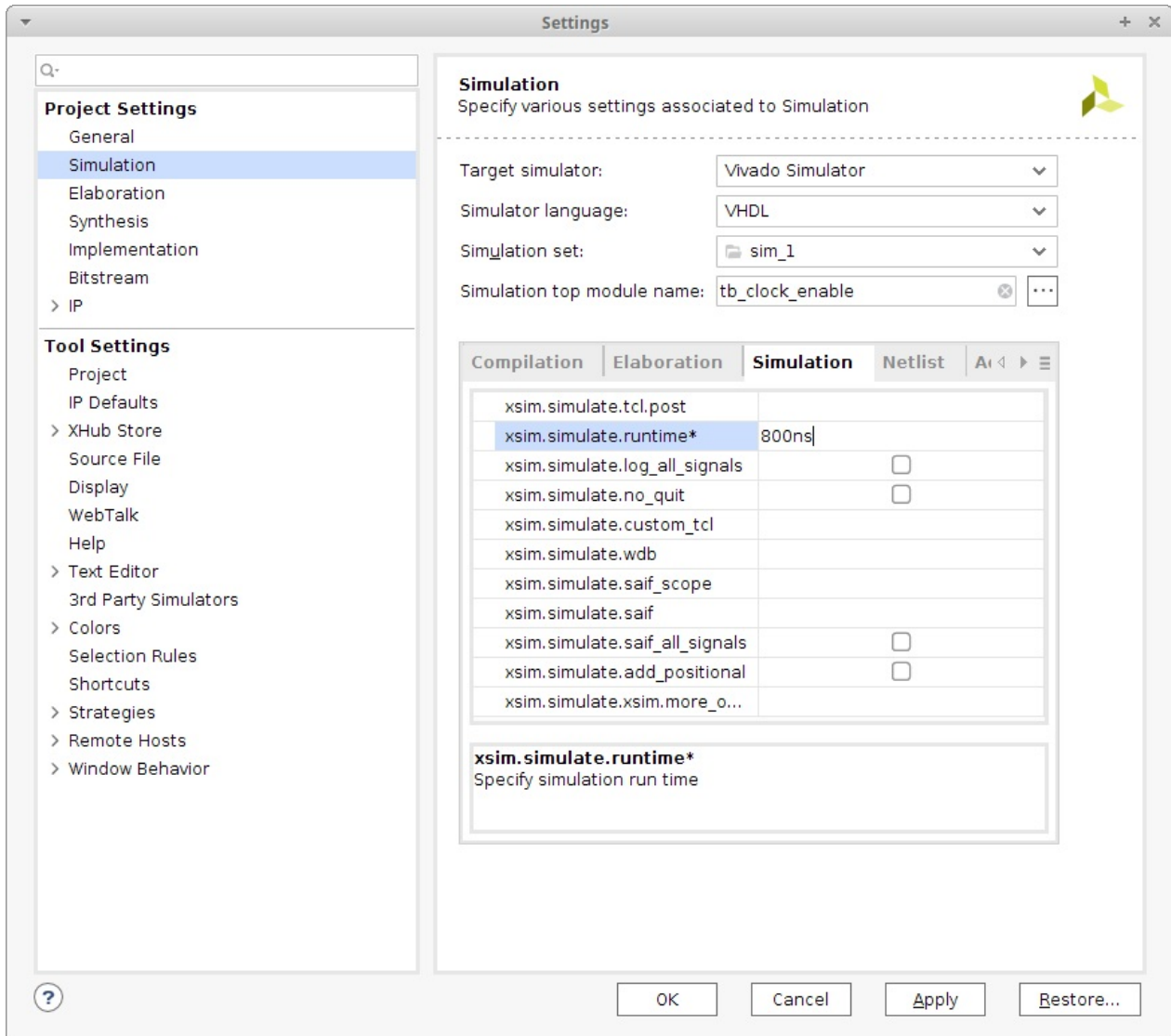

Part 3: VHDL code for bidirectional binary counter


[Bidirectional counters](#), also known as Up/Down counters, are capable of counting in either direction through any given count sequence and they can be reversed at any point within their count sequence by using an additional control input as shown below.

Perform the following steps to simulate the bidirectional N-bit counter.

- Create a new design source `cnt_up_down` in your project.
- Open the [N-bit Up/Down binary counter example](#) and copy/paste the `design.vhd` code to your `cnt_up_down.vhd` file. Take a look at the new parts of the VHDL source code.


Note that an internal `s_cnt_local` signal is used to implement the counter. This is because the **output** port `cnt_o` cannot be read and therefore the operation `cnt_o + 1` cannot be performed. Also note that local value must be retyped to the output port.

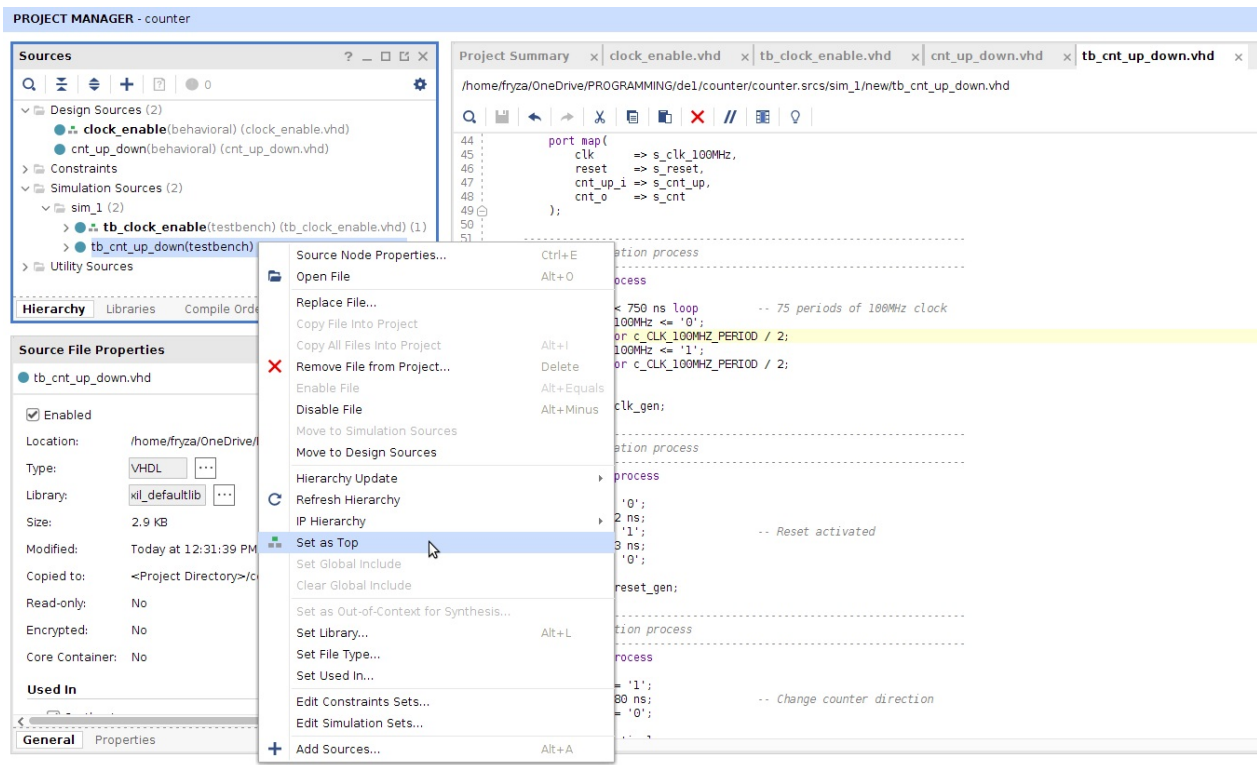- Create a simulation source `tb_cnt_up_down`, copy/paste the `testbench.vhd` code.
- Change the testbench you want to simulate, right click to file name and select **Set as Top**. Run the simulation. Verify the meaning of the constant `c_CNT_WIDTH` and reset generation process.



5. Complete architecture of the counter, make it bidirectional, and simulate again.

Note that for any vector, it is possible to change the numeric system in the simulation which represents the current value. To do so, right-click the vector name (here `s_cnt[4:0]`) and select **Radix > Unsigned Decimal** from the context menu. You can change the vector color by **Signal Color** as well.

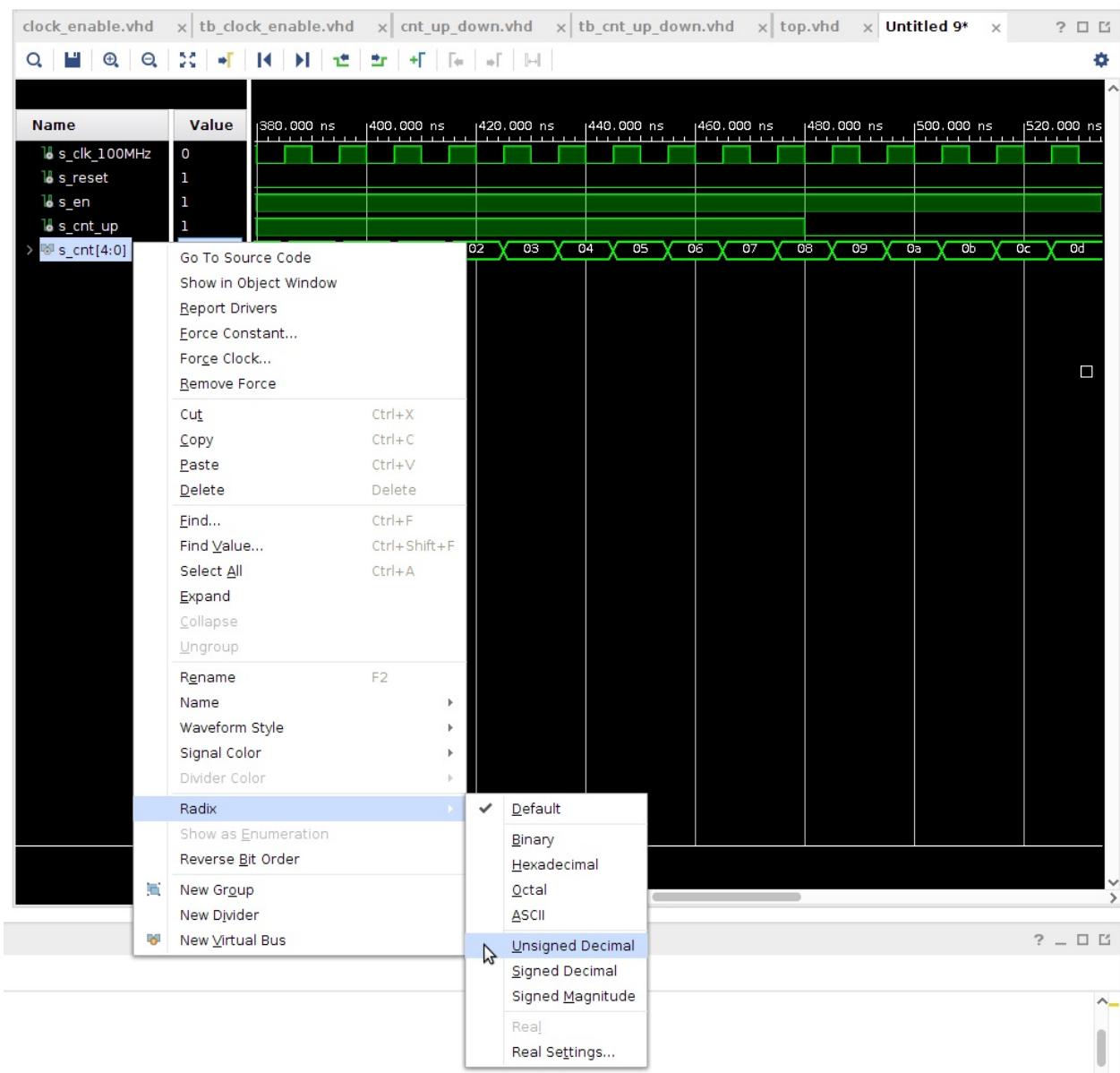

Part 4: Top level VHDL code

Perform the following steps to implement the 4-bit bidirectional counter on the Nexys A7 board.

1. Create a new design source `top` in your project.
2. Use **Define Module** dialog and define I/O ports of entity `top` as follows.

Port name	Direction	Type	Description
CLK100MHz	input	std_logic	Main clock
BTNC	input	std_logic	Synchronous reset
SW	input	std_logic_vector(1 - 1 downto 0)	Counter direction
LED	output	std_logic_vector(4 - 1 downto 0)	Counter value LED indicators
CA	output	std_logic	Cathod A
CB	output	std_logic	Cathod B
CC	output	std_logic	Cathod C
CD	output	std_logic	Cathod D
CE	output	std_logic	Cathod E
CF	output	std_logic	Cathod F
CG	output	std_logic	Cathod G
AN	output	std_logic_vector(8 - 1 downto 0)	Common anode signals to individual displays

3. Use direct instantiation and define an architecture of the top level: make a copy of `clock_enable`, `cnt_up_down`, and `hex_7seg` entities. Copy source file `hex_7seg.vhd` from the previous laboratories to the `counter/counter.srcs/sources_1/new/` source folder and add it to the project.


```

-----
-- Architecture body for top level
-----

architecture Behavioral of top is
-- Internal clock enable
signal s_en : std_logic;
-- Internal counter
signal s_cnt : std_logic_vector(4 - 1 downto 0);
begin


-- Instance (copy) of clock_enable entity
clk_en0 : entity work.clock_enable
generic map(
    --- WRITE YOUR CODE HERE
)
port map(
    --- WRITE YOUR CODE HERE
);

-- Instance (copy) of cnt_up_down entity
bin_cnt0 : entity work.cnt_up_down
generic map(
    --- WRITE YOUR CODE HERE
)
port map(
    --- WRITE YOUR CODE HERE
);


-- Display counter values on LEDs
LED(3 downto 0) <= s_cnt;

-- Instance (copy) of hex_7seg entity
hex2seg : entity work.hex_7seg
port map(
    hex_i => s_cnt,
    seg_o(6) => CA,
    seg_o(5) => CB,
    seg_o(4) => CC,
    seg_o(3) => CD,
    seg_o(2) => CE,
    seg_o(1) => CF,
    seg_o(0) => CG
);
-- Connect one common anode to 3.3V
AN <= b"1111_1110";
end architecture Behavioral;

```

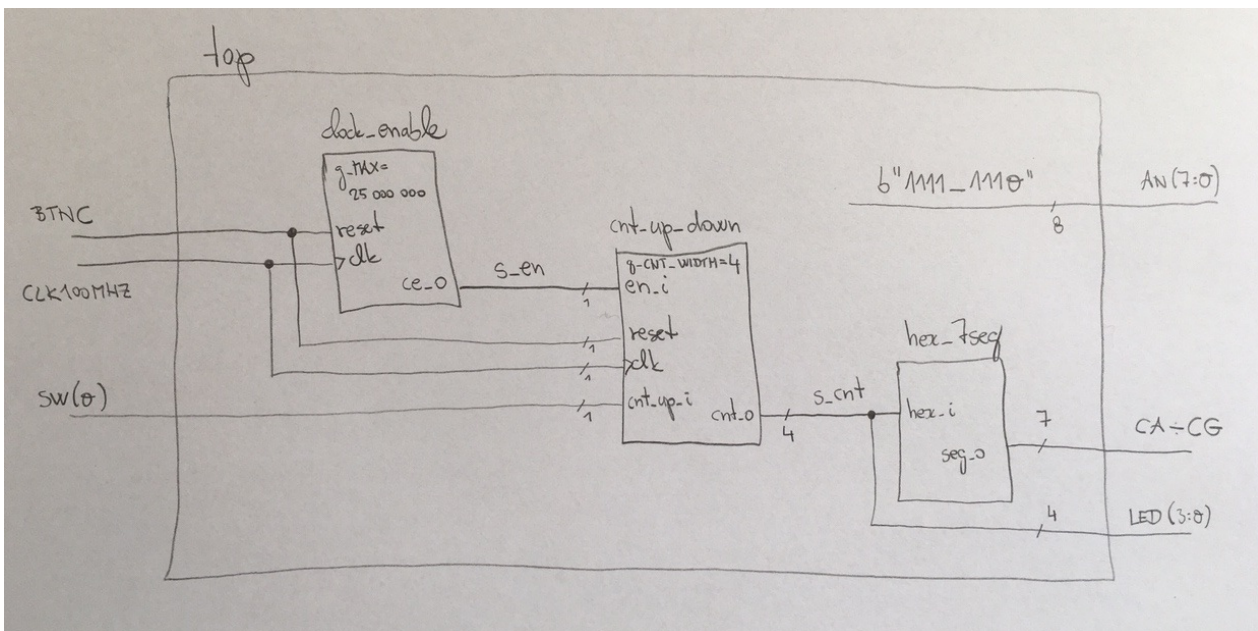

 4. Create a new [constraints XDC](#) file: nexys-a7-50t and uncomment used pins according to the top entity.
5. Compile the project and download the generated bitstream counter/counter.runs/impl_1/top.bit into the FPGA chip.
6. Test the functionality of the 4-bit counter by toggling the switch, pressing the button and observing the display and LEDs.
7. Use **IMPLEMENTATION > Open Implemented Design > Schematic** to see the generated structure.
8. Use digital oscilloscope or logic analyser and display counter values via Pmod ports. See schematic or reference manual of the Nexys A7 board and find out to which FPGA pins Pmod ports JA, JB, JC, and JD are connected.



Synchronize repositories

Use [git commands](#) to add, commit, and push all local changes to your remote repository. Check the repository at GitHub web page for changes.

Experiments on your own

1. Add a second instantiation (copy) of the counter and clock enable entities and make a 16-bit counter with a 10 ms time base. Display its value on LED(15:0).

Lab assignment

1. Preparation tasks (done before the lab at home). Submit:
 - Figure or table with connection of push buttons on Nexys A7 board,
 - Table with calculated values.
2. Bidirectional counter. Submit:
 - Listing of VHDL code of the process `p_cnt_up_down` with syntax highlighting.
 - Listing of VHDL reset and stimulus processes from testbench file `tb_cnt_up_down.vhd` with syntax highlighting and asserts,
 - Screenshot with simulated time waveforms; always display all inputs and outputs,
3. Top level. Submit:
 - Listing of VHDL code from source file `top.vhd` with all instantiations for the 4-bit bidirectional counter.
 - Image of the top layer including both counters, ie a 4-bit bidirectional counter from Part 4 and a 16-bit counter with a 10 ms time base from Part

Experiments on your own. The image can be drawn on a computer or by hand.

Prepare all parts of the assignment on a computer (not by hand), insert them in your README file `Digital-electronics-1/Labs/05-counter/README.md`, export the formatted output (not the listing in markdown language) from [HTML to PDF](#), use [BUT e-learning](#) web page and submit a single PDF file. The deadline for submitting the task is the day before the next laboratory exercise.