

Lab 8: Traffic light controller




EUROPEAN UNION
European Structural and Investment Funds
Operational Programme Research,
Development and Education



The Study of Modern and Developing Engineering BUT
CZ.02.2.69/0.0/0.0/18_056/0013325

Learning objectives

In this laboratory exercise you will implement a finite state machine (FSM) in VHDL, specifically a traffic light controller at a junction. At first, the intersection will contain only two one-way streets with a fixed time control system in which traffic lights are configured to turn on the green, yellow, and red color after a given period. Subsequently, the system will be extended with a smarter way of driving.

 

Preparation tasks (done before the lab at home)

Read the article [Implementing a Finite State Machine in VHDL](#) (parts **A Bit of Background** and **The Finite State Machine**) and understand what an FSM is.

Fill in the table with the state names and output values according to the given inputs. Let the reset has just been applied.

| | | | | | | | | | | | | | | | | |
|-----------------|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|
| Input P | 0 | 0 | 1 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 1 |
| Clock | | | | | | | | | | | | | | | | |
| State | A | | | | | | | | | | | | | | | |
| Output R | 0 | | | | | | | | | | | | | | | |

See schematic or reference manual of the Nexys board and find out the connection of two RGB LEDs. How you can control them to get red, yellow, or green colors?

| RGB LED | Artix-7 pin names | Red | Yellow | Green |
|---------|-------------------|---------|--------|-------|
| LD16 | N15, M16, R12 | 1, 0, 0 | | |
| LD17 | | | | |


Part 1: Synchronize Git and create a new folder

Run Git Bash (Windows) or Terminal (Linux), navigate to your working directory, and update local repository. Create a new working folder `Labs/08-traffic_lights`.

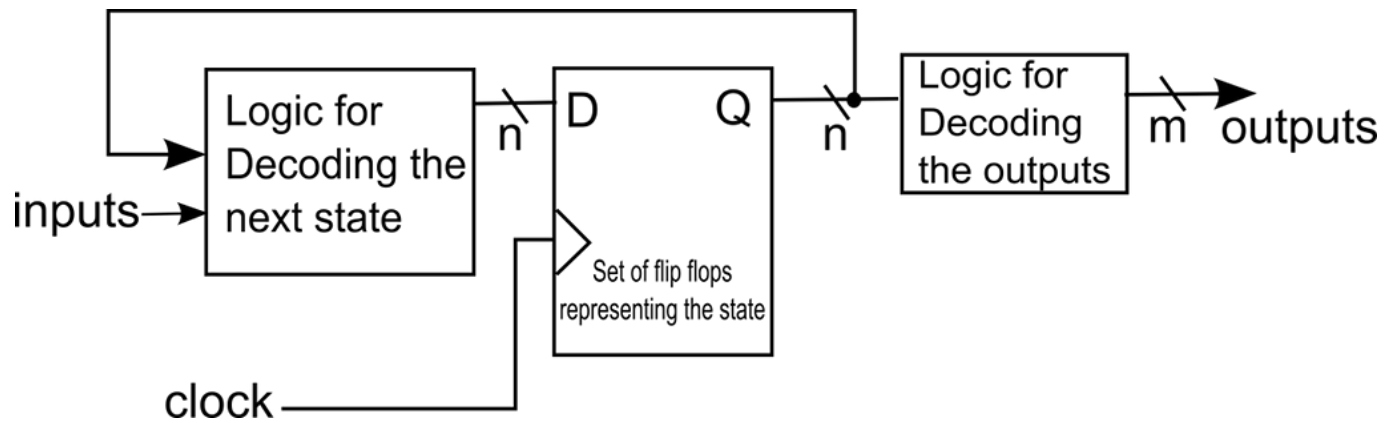Part 2: Finite State Machine (FSM)

A finite state machine (FSM) is a computation model that can be implemented with hardware or software and can be used to simulate sequential logic. There are two main types of finite state machines: the Mealy FSM and the Moore FSM. The fundamental difference between these two types lies in the management of the outputs:


- The output of the **Mealy** machine depends on the present state and inputs.
- The outputs of a **Moore** machine depend only on the present state and not on the inputs, as shown in the figure [\[1\]](#).




A common way how to represent a finite state machine is a **state diagram** which contains of:

- Circles and
- Directed arcs to the next state circles.

 Circles represent the machine states labelled with a reflecting state and for a Moore machine also with the output value [2].




 Directed arcs represent the transitions between states and they are labelled with input/output pair for a Mealy machine and with input for a Moore machine.



MOORE Machine:
Outputs on States

Inputs/outputs

 

MEALY Machine:
Outputs on Transitions

Arcs leaving a state must be:

(1) **mutually exclusive**

- can't have two choices for a given input value

(2) **collectively exhaustive**

- every state must specify what happens for each possible input combination. "Nothing happens" means arc back to itself.

Part 3: VHDL code for traffic light controller

Let an intersection contains two one-way streets with a fixed time control system in which traffic lights are configured to turn on the green, yellow, and red color after a given period. If it is red in one direction on the traffic light, it is green in the other, and green in the first direction can only occur when it is red in the other direction, etc.

The exercise is inspired by the references [3], [1], [4], while several changes have been made to preserve the programming style from the previous exercises, such as:

- Use `numeric_std` package instead of `IEEE.STD_LOGIC_unsigned`,
- Types for internal signal/constants changed from `STD_LOGIC_VECTOR(3 downto 0)` to `unsigned`,
- Edge detector `clk'event and clk = '1'` changed to `rising_edge(clk)`.

Perform the following steps to model the traffic light controller.

1. Create a new Vivado RTL project `traffic` in your `Labs/08-traffic_lights` working folder.
2. Create a VHDL source file `tlc` for the traffic light controller circuit.
3. Choose default board: `Nexys A7-50T`.
4. Open the `Traffic light controller` example and copy/paste the `design.vhd` code to your `tlc.vhd` file.
5. Skip this step if you are only performing a simulation and not a real hardware implementation. Copy source file of clock enable circuit from previous labs to `traffic/traffic.srcs/sources_1/new/` folder and add it to the project.

6. Complete the traffic light code according to the following description.

The controller contains six states and sets the semaphore outputs according to the following table. It remains in each of the states for a certain time.

| Current state | Direction South | Direction West | Delay |
|---------------|-----------------|----------------|-------|
| STOP1 | red | red | 1 sec |
| WEST_GO | red | green | 4 sec |
| WEST_WAIT | red | yellow | 2 sec |
| STOP2 | red | red | 1 sec |
| SOUTH_GO | green | red | 4 sec |
| SOUTH_WAIT | yellow | red | 2 sec |

Draw a state diagram according to the table.

In VHDL it is possible to define a new data type, which contains the names of our states.

```
-- Define the states
type t_state is (STOP1, WEST_GO, WEST_WAIT,
                 STOP2, SOUTH_GO, SOUTH_WAIT);
-- Define the signal that uses different states
signal s_state : t_state;
```

The FSM function is divided into two processes, where the first is sequential and it entirely controls state changes by CASE statement. The second is a combinatorial process, it is sensitive to state changes, and sets the output signals accordingly. This is an example of a Moore state machine because the output is set based on the active state. FSM behavior can be written in one to three processes. The differences between these approaches are described in detail [here](#).

Complete CASE/WHEN statements in both sequential and combinatorial processes.

Sequential process:

```

-----
-- p_traffic_fsm:
-- The sequential process with synchronous reset and clock_enable
-- entirely controls the s_state signal by CASE statement.
-----
p_traffic_fsm : process(clk)
begin
    if rising_edge(clk) then
        if (reset = '1') then          -- Synchronous reset
            s_state <= STOP1 ;          -- Set initial state
            s_cnt   <= c_ZERO;          -- Clear all bits

        elsif (s_en = '1') then
            -- Every 250 ms, CASE checks the value of the s_state
            -- variable and changes to the next state according
            -- to the delay value.
            case s_state is

                -- If the current state is STOP1, then wait 1 sec
                -- and move to the next GO_WAIT state.
                when STOP1 =>
                    -- Count up to c_DELAY_1SEC
                    if (s_cnt < c_DELAY_1SEC) then
                        s_cnt <= s_cnt + 1;
                    else
                        -- Move to the next state
                        s_state <= WEST_GO;
                        -- Reset local counter value
                        s_cnt   <= c_ZERO;
                    end if;

                when WEST_GO =>

                    -- WRITE YOUR CODE HERE

                -- It is a good programming practice to use the
                -- OTHERS clause, even if all CASE choices have
                -- been made.
                when others =>
                    s_state <= STOP1;

            end case;
        end if; -- Synchronous reset
    end if; -- Rising edge
end process p_traffic_fsm;

```

Combinatorial process:

```

-----
-- p_output_fsm:
-- The combinatorial process is sensitive to state changes, and sets
-- the output signals accordingly. This is an example of a Moore
-- state machine because the output is set based on the active state.
-----
p_output_fsm : process(s_state)
begin
    case s_state is
        when STOP1 =>
            south_o <= "100";    -- Red (RGB = 100)
            west_o  <= "100";    -- Red (RGB = 100)
        when WEST_GO =>

            -- WRITE YOUR CODE HERE

        when others =>
            south_o <= "100";    -- Red
            west_o  <= "100";    -- Red
    end case;
end process p_output_fsm;

```

Part 4: Traffic light controller simulation

Perform the following steps to simulate traffic light controller.

1. Create a VHDL simulation source `tb_tlc`, copy/paste the `testbench.vhd` code from [EDA Playground example](#). Note that the maximum value of clock enable circuit is set to 1 for the simulation, ie the traffic light controller changes its state with a frequency of 100 MHz and not 4 Hz.
2. Change the duration of simulation to 10000ns in Vivado menu **Tools > Settings... > Simulation > Simulation**.
3. Run the simulation, and verify that the controller works correctly (reset, timing, output lights, states).

Part 5: Top level VHDL code

Perform the following steps to implement the traffic light controller on the Nexys A7 board.

1. Create a new design source `top` in your project.
2. Define an entity `top` as follows.

| Port name | Direction | Type | Description |
|-----------|-----------|-----------|-------------------|
| CLK100MHZ | input | std_logic | Main clock |
| BTNC | input | std_logic | Synchronous reset |
| LED16_R | output | std_logic | Red1 |

| Port name | Direction | Type | Description |
|-----------|-----------|-----------|-------------|
| LED16_G | output | std_logic | Green1 |
| LED16_B | output | std_logic | Blue1 |
| LED17_R | output | std_logic | Red2 |
| LED17_G | output | std_logic | Green2 |
| LED17_B | output | std_logic | Blue2 |

3. Create a new [constraints XDC](#) file: `nexys-a7-50t` and uncomment used pins according to the entity.
4. Use direct instantiation and define an architecture of the top level.

```

-----
-- Architecture body for top level
-----
architecture Behavioral of top is

begin
    -----
    -- Instance (copy) of tlc entity
    tlc : entity work.tlc
        port map(
            clk    => CLK100MHZ,
            reset  => BTNC,
            --- WRITE YOUR CODE HERE
        );

end architecture Behavioral;

```


5. Compile the project and download the generated bitstream `traffic/traffic.runs/impl_1/top.bit` into the FPGA chip.
6. Observe the functionality of the traffic light controller.
7. Use **IMPLEMENTATION > Open Implemented Design > Schematic** to see the generated structure.

Synchronize repositories

Use [git commands](#) to add, commit, and push all local changes to your remote repository. Check the repository at GitHub web page for changes.

Experiments on your own

 1. Follow the [exercise inspired by prof. Jon Valvano](#) from University of Texas and desing an enhanced traffic light controller for the intersection of two equally busy one-way streets. The controller using two sensors and two traffic lights in three colors . Two sensors detects the presence of cars in each direction and the goal is to maximize traffic flow, minimize waiting time at a red light, and avoid accidents.



Traffic Lights Intersection

Arduining.com

Propose your own state table and draw a state diagram of this smart controller including delays. Use on-board slide switches to emulate two sensors and implement the traffic light controller on the Nexys A7 board.

Lab assignment

1. Preparation tasks (done before the lab at home). Submit:

- Completed state table,
- Figure with connection of RGB LEDs on Nexys A7 board and completed table with color settings.

2. Traffic light controller. Submit:

- State diagram,
- Listing of VHDL code of sequential process `p_traffic_fsm` with syntax highlighting,
- Listing of VHDL code of combinatorial process `p_output_fsm` with syntax highlighting,
- Screenshot(s) of the simulation, from which it is clear that controller works correctly.

3. Smart controller. Submit:

- State table,
- State diagram,
- Listing of VHDL code of sequential process `p_smart_traffic_fsm` with syntax highlighting.

Prepare all parts of the assignment on a computer (not by hand), insert them in your README file `Digital-electronics-1/Labs/08-traffic_lights/README.md`, export the formatted output (not the listing in

markdown language) from [HTML to PDF](#), use [BUT e-learning](#) web page and submit a single PDF file. The deadline for submitting the task is the day before the next laboratory exercise.

References

1. David Williams. [Implementing a Finite State Machine in VHDL](#)
2. MIT OpenCourseWare. [L06: Finite State Machines](#)
3. LBEbooks, Lesson 92 - Example 62: [Traffic Light Controller](#)
4. VHDLwhiz, [One-process vs two-process vs three-process state machine](#)
5. Jon Valvano. [Traffic Light , Finite State Machine with Arduino](#)